

# Impact of Shunt Reactor Bank Switching on Transformer Neutral Geomagnetic Induced Current (GIC) Monitoring

---

**Larry Anderson**  
**Cigre GOTF – Houston, TX**  
**October 20, 2014**

# Background

---

- **AEP started installing GIC monitors in 2012**
- **Currently 13 EHV transformer installations are monitored with more on the way**
- **Presently most installations are on 765 kV autotransformers (10 out of 13 installations)**
- **AEP utilizes switched shunt reactors at specific locations on it's EHV system to assist with voltage regulation**
- **Shortly after monitor installation large DC transients were observed at locations with switched shunt reactors on site or nearby**



# Background Cont'd

---

- **Initially reactor bank switching was overlooked as a source of the DC transient current**
- **Only after considering what type of transient events could produce such DC transients, were the switched shunt reactor banks investigated more closely**
- **After looking at reactor breaker closing times in relation to the DC neutral transients, it was observed that they coincided**
- **At this point it was decided to study these transients more closely to understand their true nature**

# Observed Transients



## ● Sullivan Transformer #1

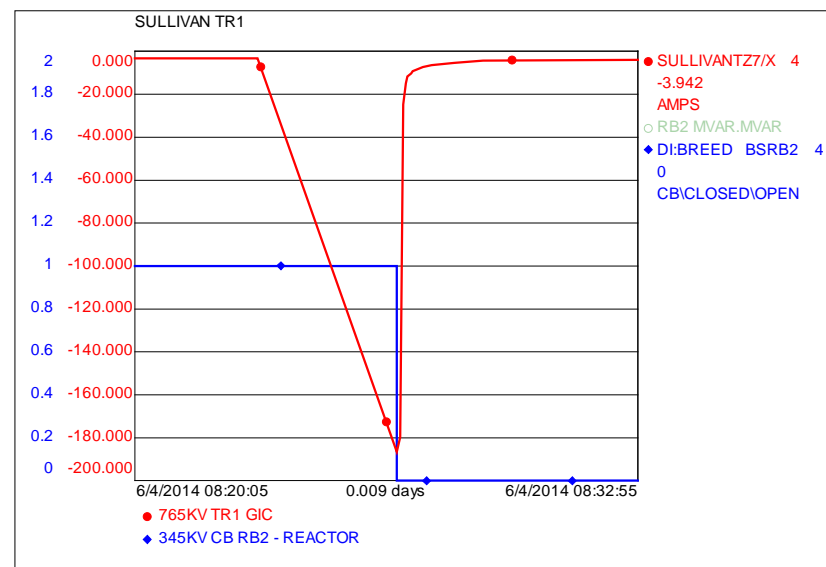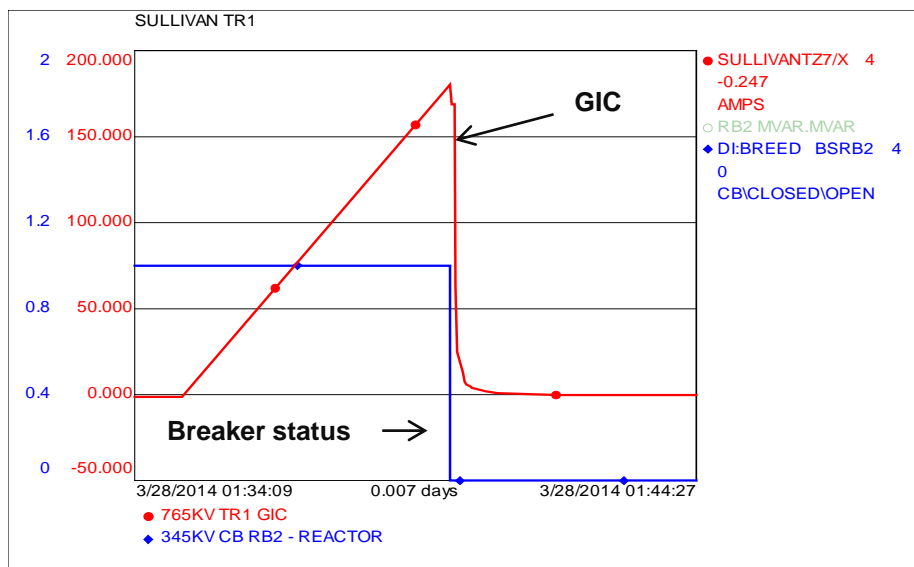

- Data from AEP's SCADA system
- Low sampling rate
- Modified by data historian (swinging door compression)

# Observed Transients Cont'd


## ● Marysville Transformer #3

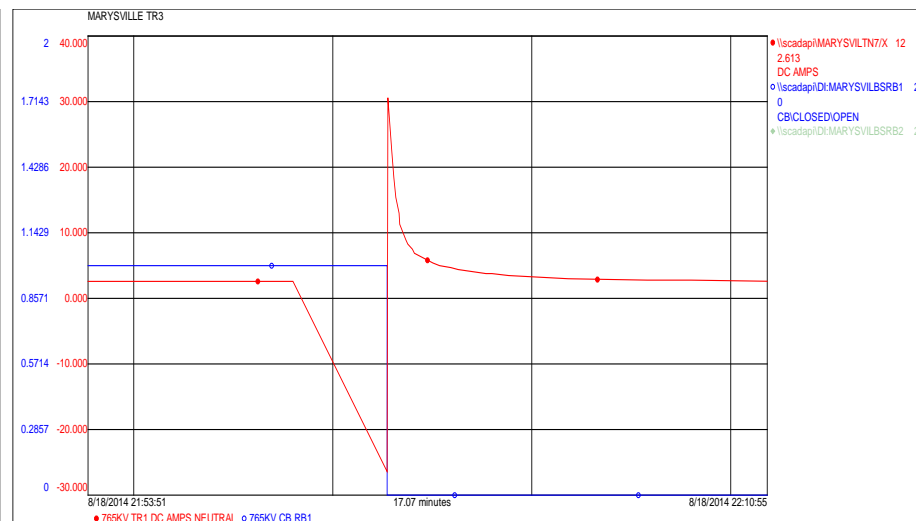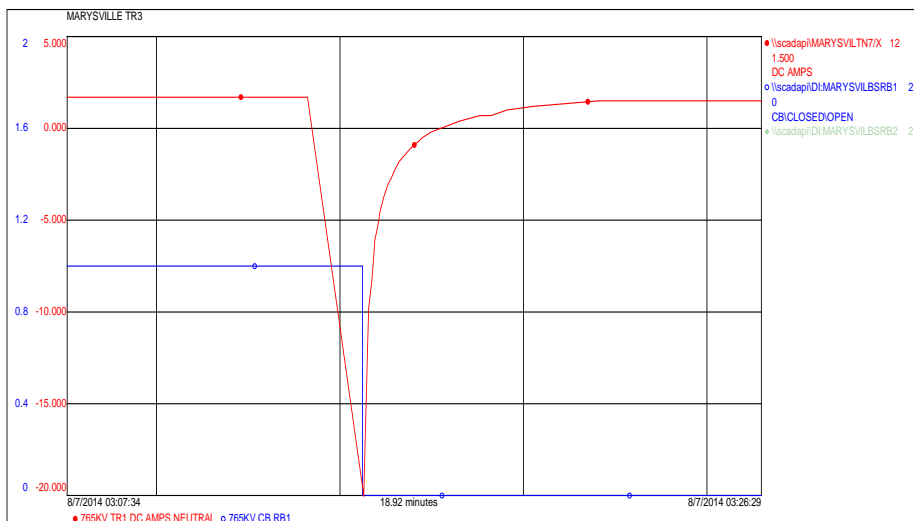

- Red curves are the currents recorded by GIC monitors
- Blue curves are reactor breaker status – “1” indicates open, “0” indicates closed
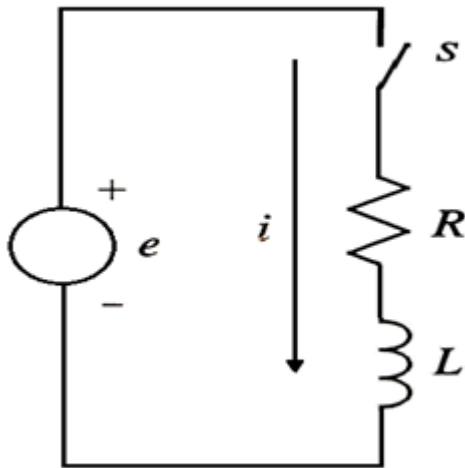
# Reactor Bank Switching Transients

- **Easily understood by analyzing the switching response of a simple RL circuit**



Where  $e = E_m \sin(\omega t + \alpha)$

Solving for  $i$ :

$$i = Ke^{-\frac{R}{L}(t-t_s)} + \frac{E_m}{Z} \sin(\omega t + \alpha - \varphi) \quad (1)$$

Where  $Z = \sqrt{R^2 + \omega^2 L^2}$


$$\varphi = \tan^{-1} \left( \frac{\omega L}{R} \right)$$

$\alpha = \text{voltage phase angle}$

$K$  is a constant such that the current at  $t_s+$  equals the


current at  $t_s-$  :  $K = -\frac{E_m}{Z} \sin(\omega t_s + \alpha - \varphi)$
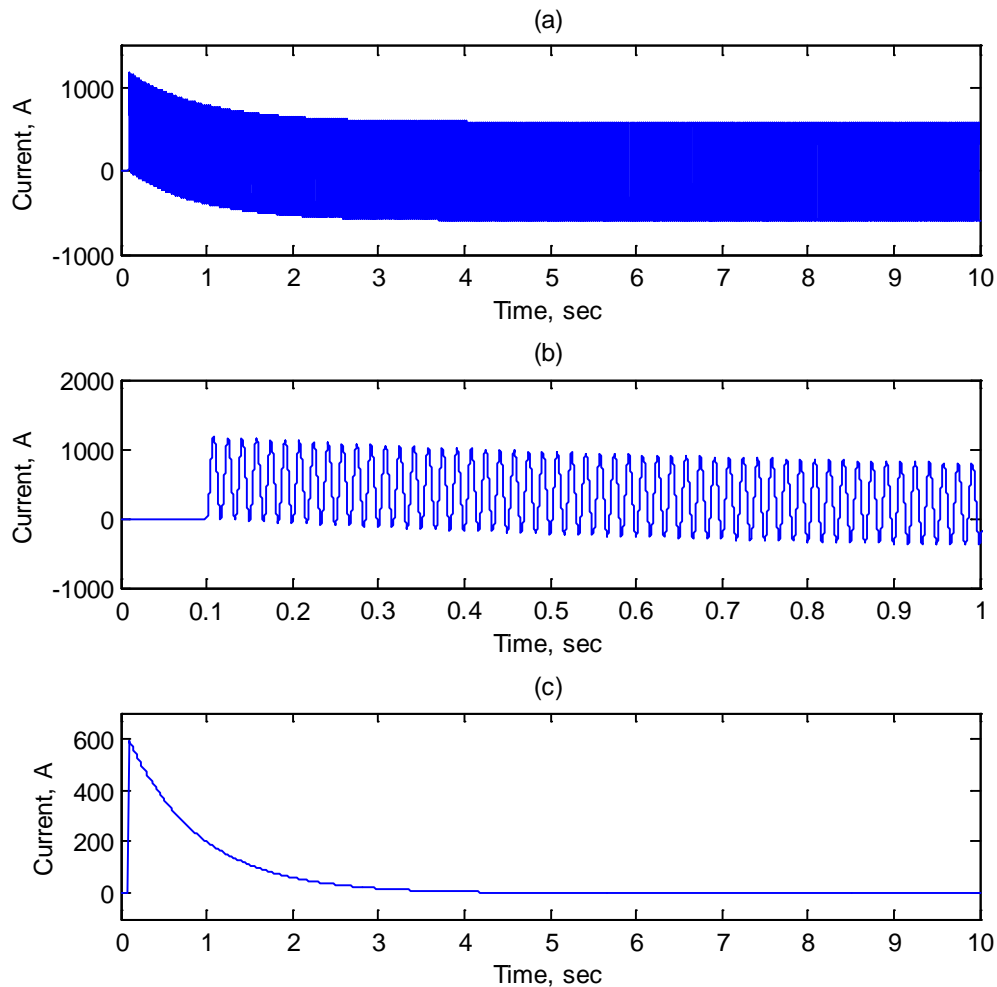
# Reactor Bank Switching Transients Cont'd




- **Current calculated with equation (1) on previous slide**
- **Reactor switching response is similar to system fault response**
- **DC offset keeps the current just after switching the same as the current just prior to switching**
- **AC current rides on top of DC offset**
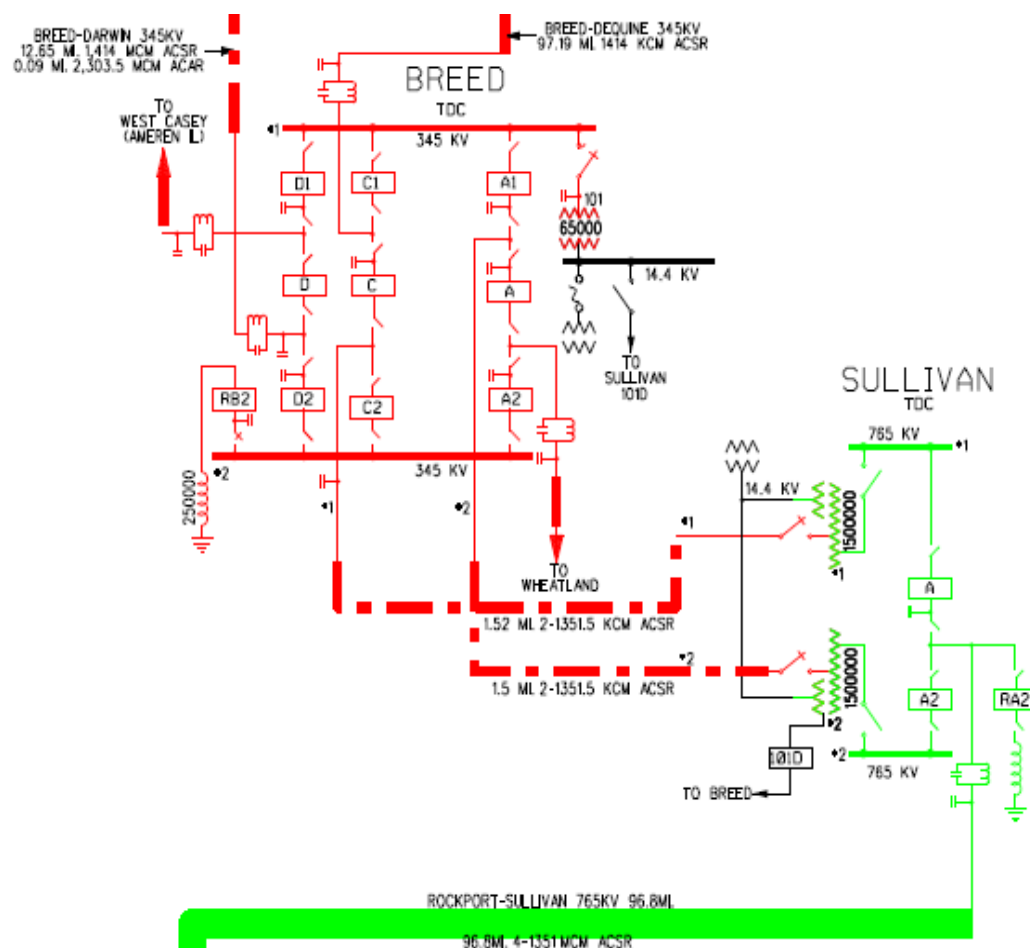
# Single Line Diagram of System Under Study






# PSCAD Model and Simulations

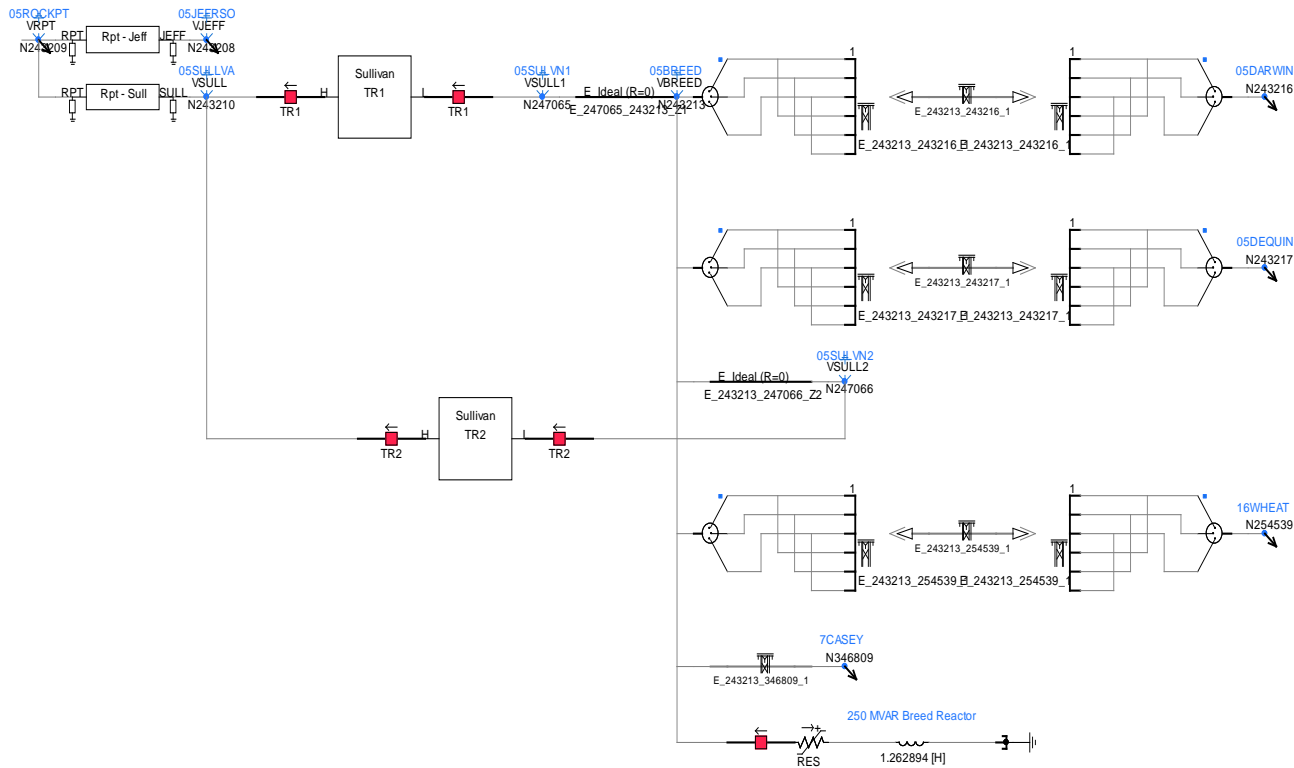

- The system was modeled in detail at least one bus away from the Sullivan 765 kV and Breed 345 kV buses
- The breaker used to switch the reactor was modeled with a pole closing span of 4.16 ms
- All transmission lines utilized full frequency dependent models
- Impact of breaker, point-on-wave closing time was investigated
- Impact of reactor resistance (X/R ratio) was investigated
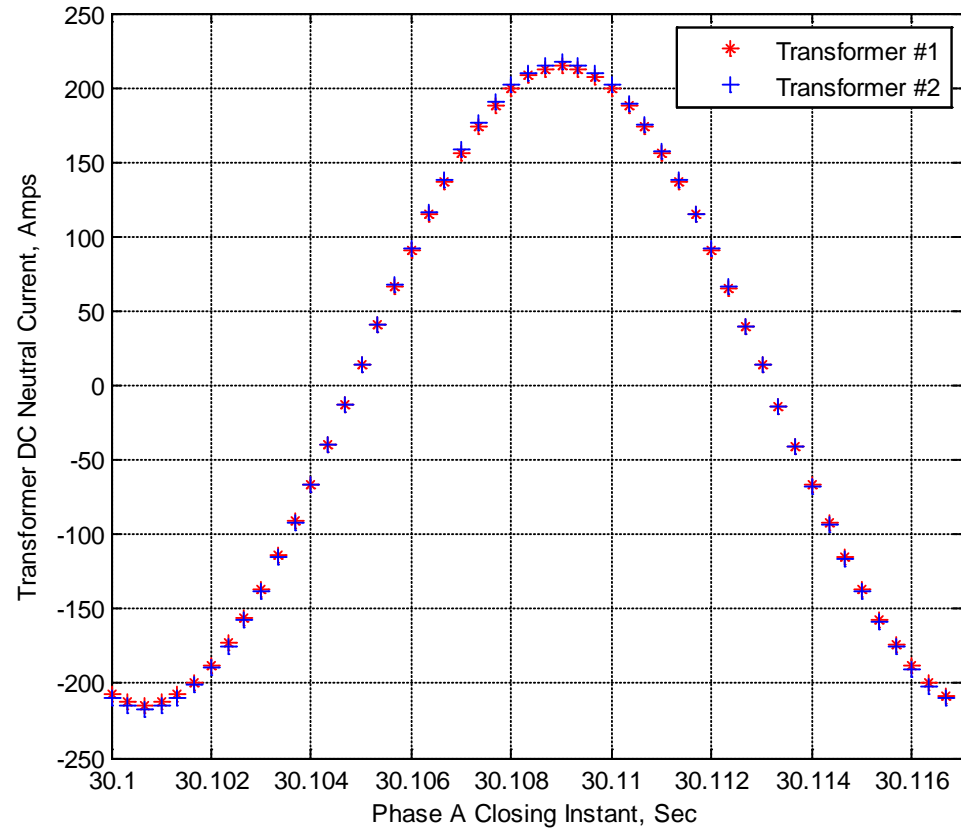
# Simulation Results


Sullivan Transformer 1 and 2 DC Neutral Current as a Function of Breed Reactor Closing Instant



- **Peak DC neutral current is a function of the point-on-wave closing instant of the reactor breaker**
- **Peak DC neutral current in the simulations ranged from approximately 200 A into the transformers to approximately 200 A out of the transformers (approx. 400 A range)**
- **This variation was solely due to the point-on-wave closing instant of the reactor breaker**
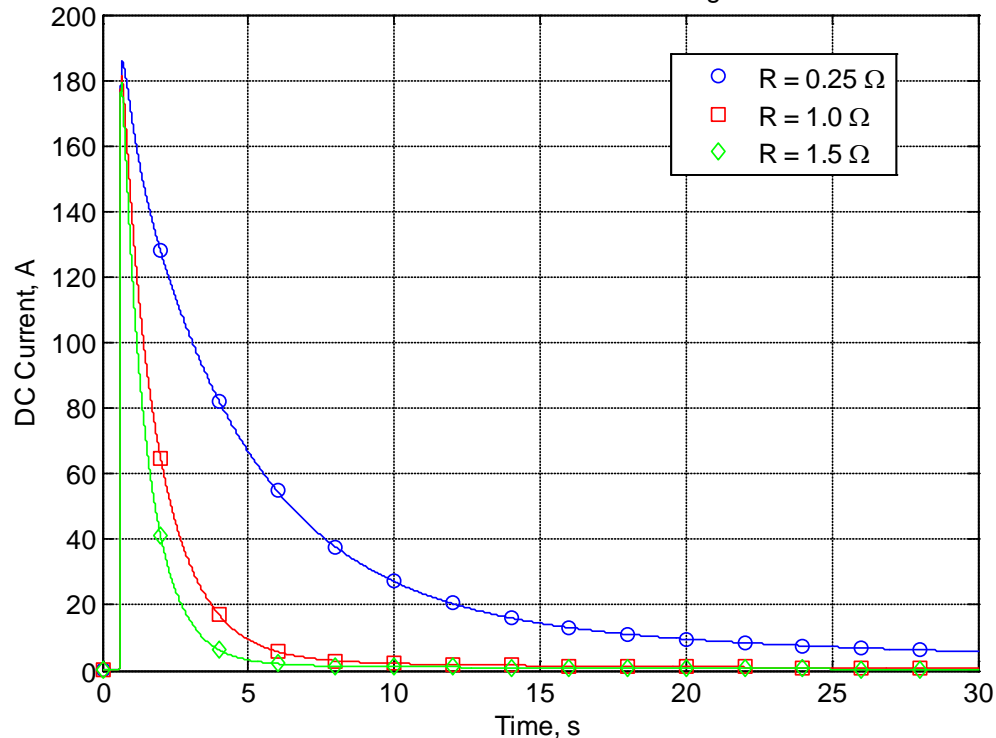
# Simulation Results Cont'd

Sullivan Auto T1 DC Neutral Current for Breed Reactor Closing - Various Reactor Resistances



- **DC neutral current exhibits exponential decay typical of inductive circuits**
- **Time constant of decay is the ratio of reactor plus system inductance over reactor plus system resistance**
- **Time constants for the Sullivan system were typically in the range of seconds (approximately 1 - 10 seconds)**

# Conclusion

---

- **Switching of inductive devices inherently produces electrical transients**
  - Seen in both the voltage and current
  - Result in a decaying DC component in the current
- **DC current:**
  - Is a function of the point on the voltage wave that each circuit breaker pole closes
  - Will typically be different in each phase due 120° electrical separation
  - Add in neutral connections of wye-grounded transformers
  - Appear as a DC current transient to monitoring devices
- **Effects of switched shunt reactor banks must be considered when implementing GIC monitoring on nearby transformers**

---

**Questions ?**