

# Dominion Energy®

## Real-Time Testing of STATCOM and SVC Controllers

Rebecca Rye

# Acknowledgements



Kyle Thomas

Dr. Hung-Ming Chou



Chathura Patabandi

# SIEMENS

Murat Sezer

Arnold Rischer



Hezi Touaf

Adam Sparacino


# Power Electronic Devices in Power Systems

Solar farm



**H**igh **V**oltage  
**D**irect **C**urrent  
(HVDC)


Wind farm

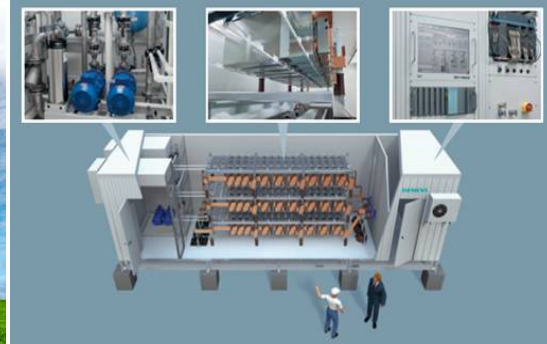


SVC & STATCOM  
(for voltage  
regulation)

# Types of Shunt Devices for Voltage Regulation


**Fixed Cap/  
Fixed Reactor**

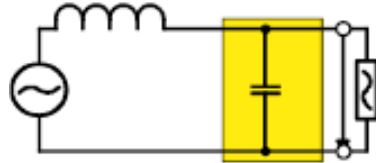

**SVC**

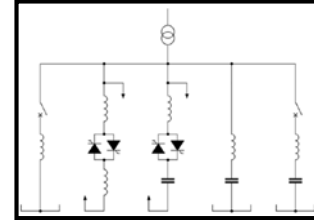


**STATCOM**

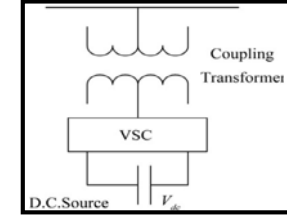

<b>Switch mechanism</b>	Mechanical	Power Electronics	Power Electronics
<b>Reactive power (Q) control method</b>	Manual / Automatic	Automatic	Automatic
<b>Q change step size</b>	Large	Small	Small
<b>Both capacitive &amp; inductive?</b>	No	Yes	Yes
<b>Need harmonic filter?</b>	No	Large filter	Small filter

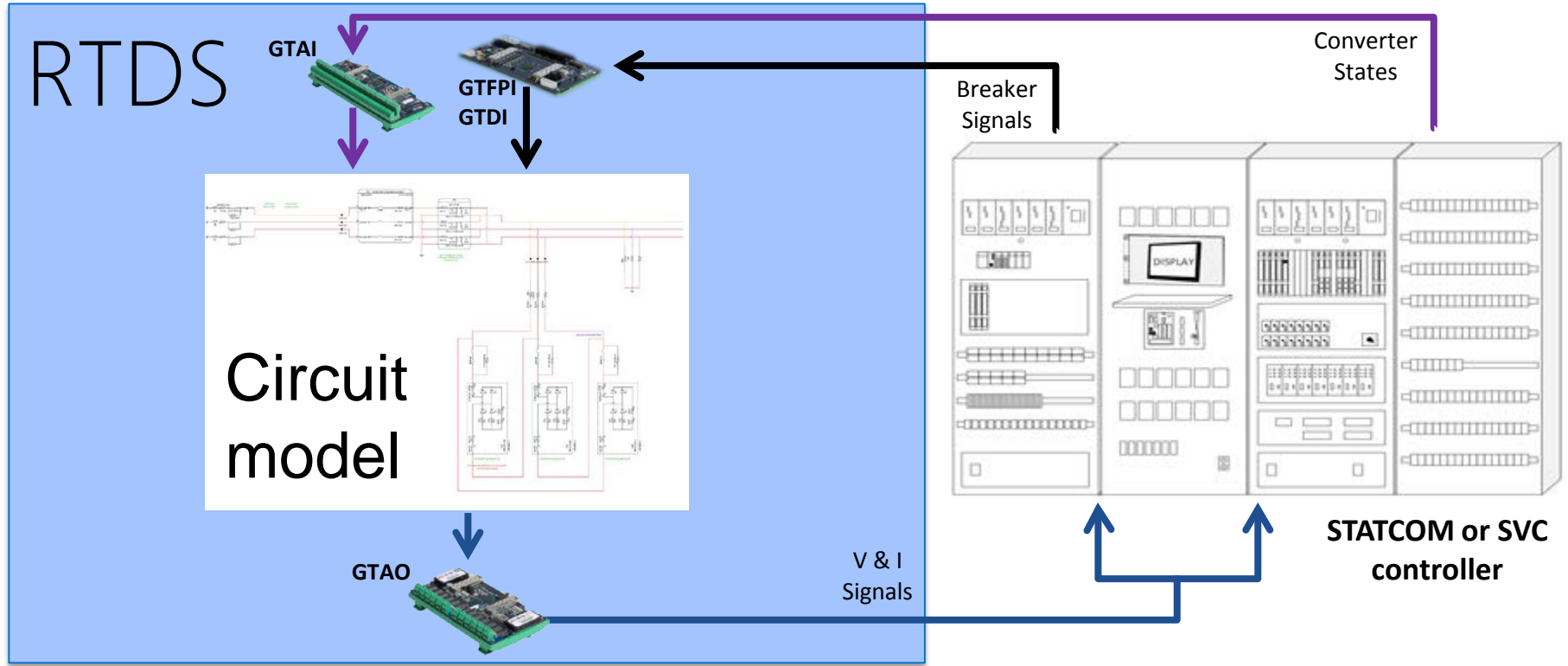
# Hardware-in-the-Loop (HIL) Experiments on RTDS






# Introduction to the STATCOM
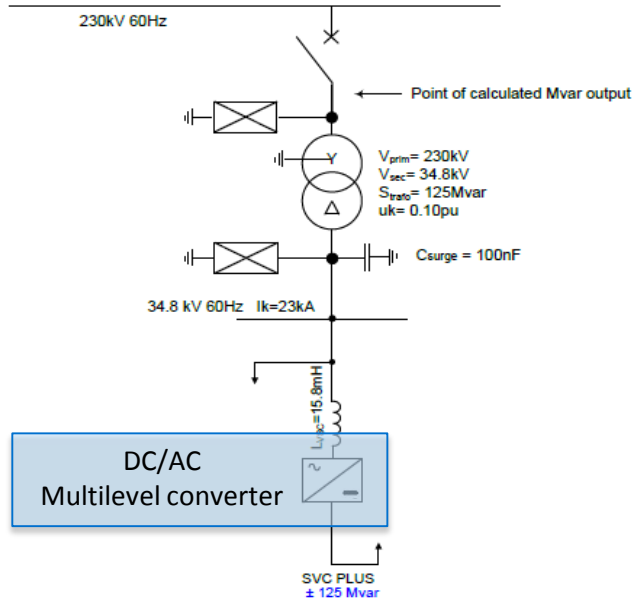
## Static Synchronous Compensator


A regulating device that can act as either a source or sink of reactive power using IGBTs



2-level converter

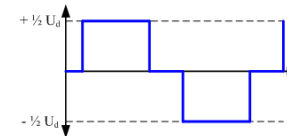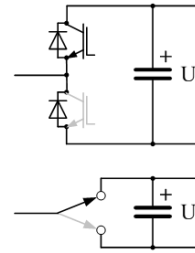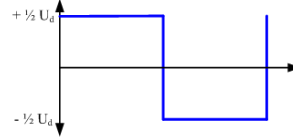


3-level converter

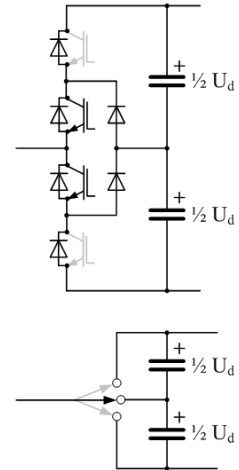

# Introduction to the STATCOM

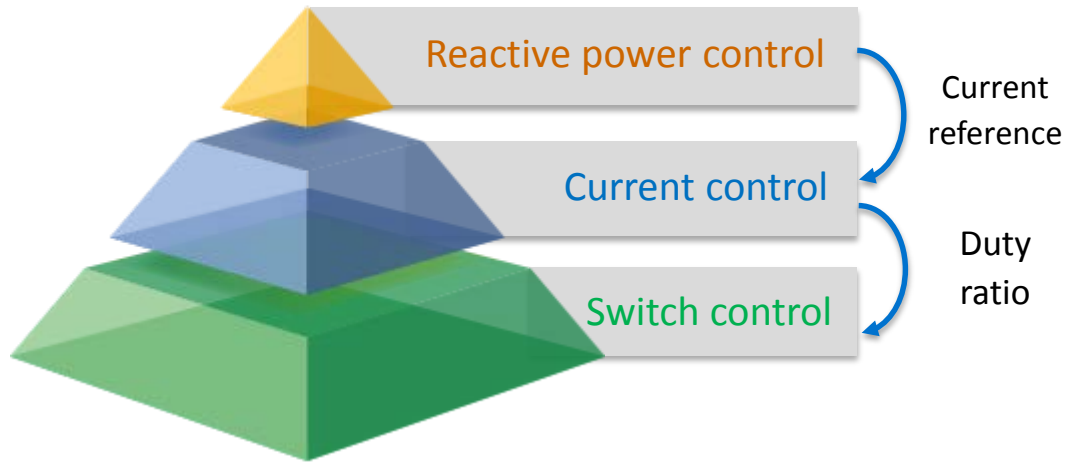
## Static Synchronous Compensator

A regulating device that can act as either a source or sink of reactive power



### Reactive power control

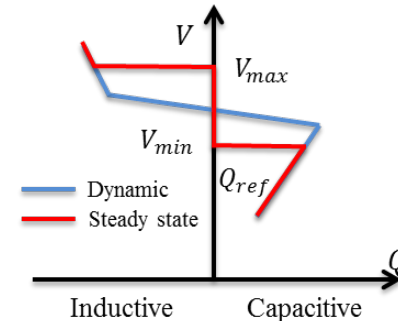- (1) Fixed Q mode / Manual mode
- (2) Voltage Control Mode




# STATCOM RTDS Tests

## Functional Performance Tests (FPT)

- Operational behavior

- ✓ Start up and shut down
- ✓ V/Q characteristic
- ✓ Gain controller test
- ✓ Stability controller
- ✓ Redundancy switchover


## System diagram

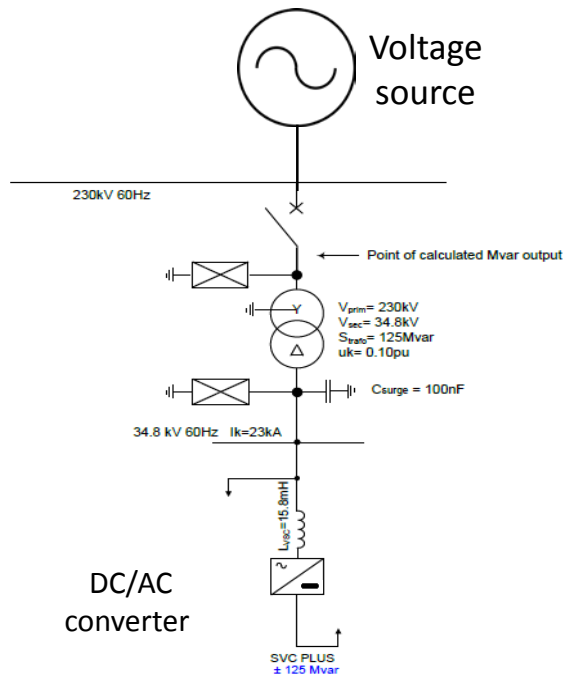




# STATCOM RTDS Tests
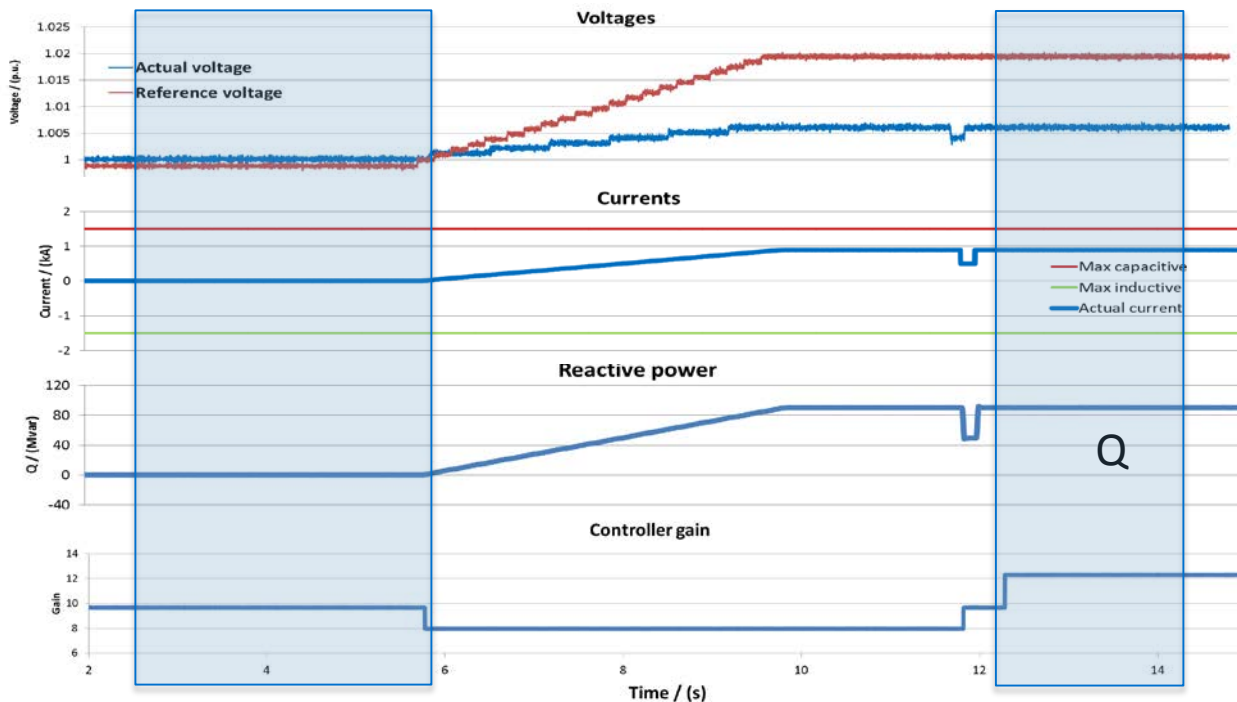
## Mode transfer from fixed Q (FQM) to voltage control (VCM)



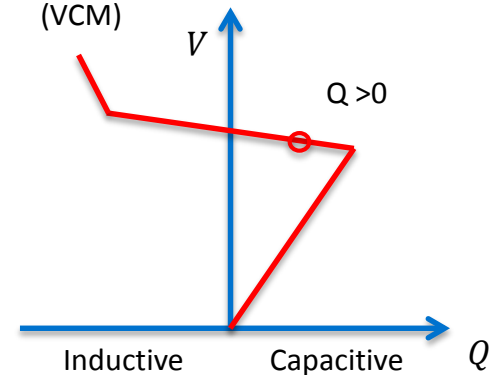- (1) In fixed Q (FQM)  $Q$  reference = 0
- (2) Mode transfer
- (3) Gain of VCM controller is adjusted
- (4) Operation point in voltage control (VCM)




# STATCOM RTDS Tests

## Dynamic Performance Tests (DPT)

- Transient behavior


- ✓ Faults
- ✓ Load switching
- ✓ External transformer energization

System diagram

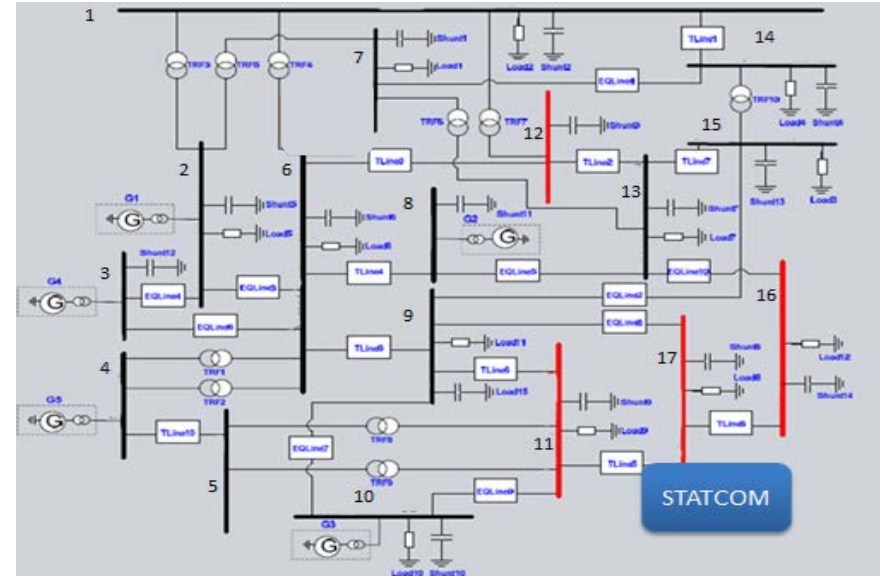
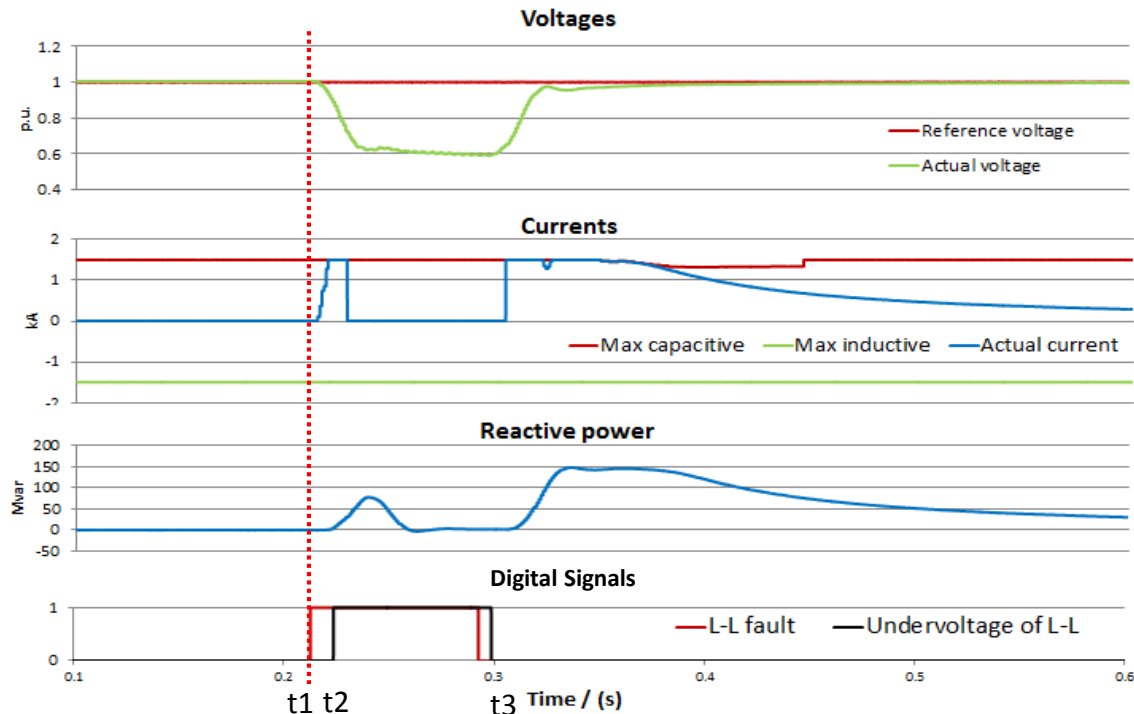
# STATCOM RTDS Tests

Dynamic performance of STATCOM in phase to phase fault



t1 : Line to line fault

t2 : STATCOM blocked  
because of undervoltage


t3 : Fault is clear  
STATCOM is unblocked

# Introduction to the SVC
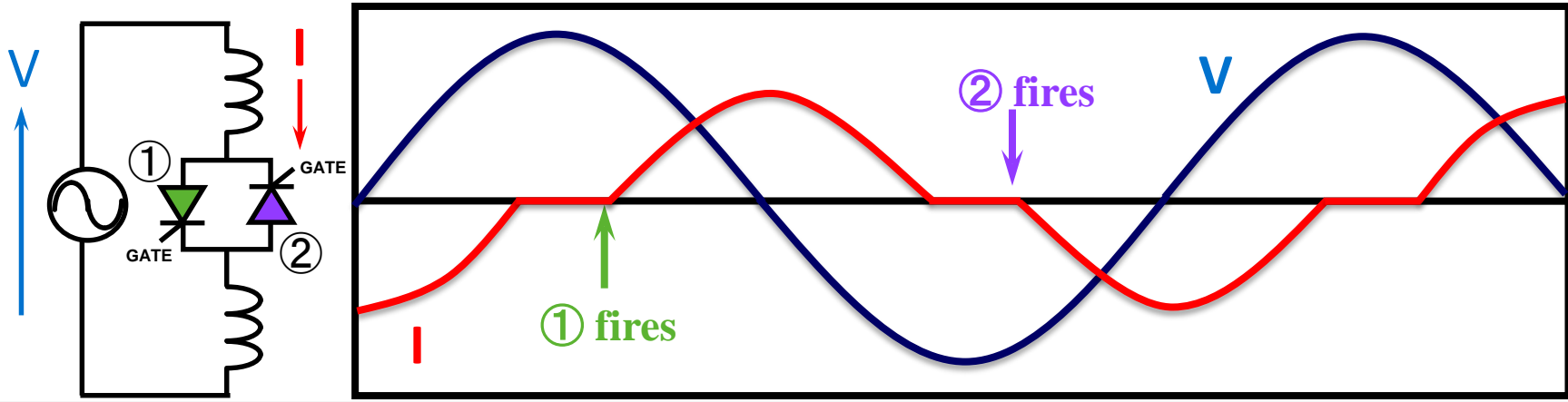
## Static VAR Compensator

A device which regulates voltage by injecting or removing reactive power using:


- TCR: Thyristor Controlled Reactor
- TSC: Thyristor Switched Capacitor



# Introduction to the SVC

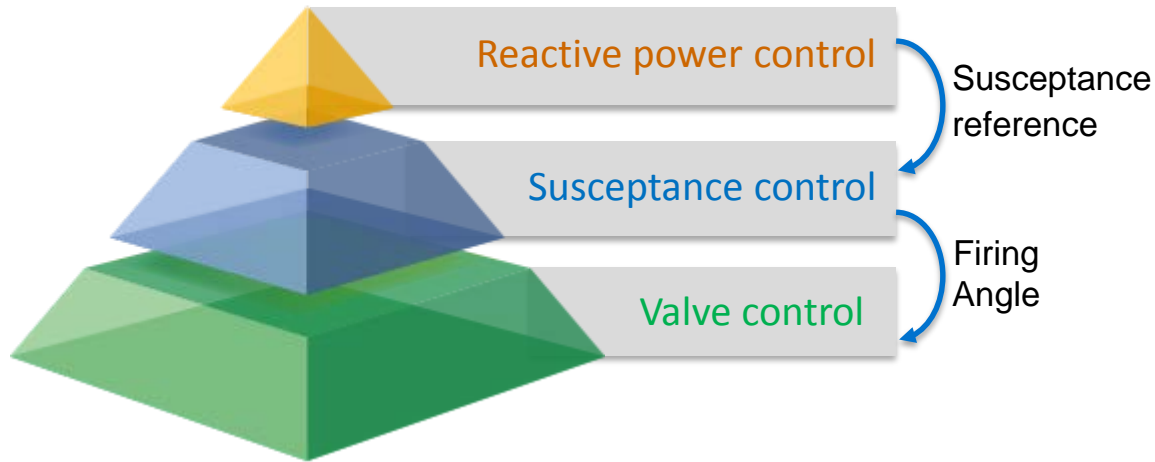
## Static VAR Compensator

A device which regulates voltage by injecting or removing reactive power



### Reactive power control

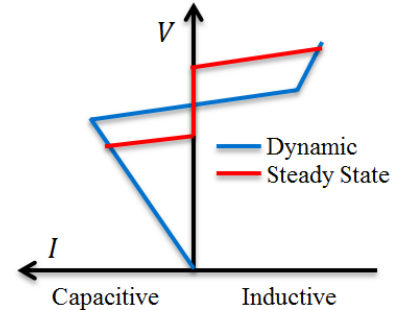- (1) Susceptance Control (Q-Mode)
- (2) Voltage Regulator (AVR)




# SVC RTDS Tests

## System Verification Tests


- Operation and static/dynamic characteristics

- ✓ Start up & shut down
- ✓ Protection
- ✓ V-I characteristics
- ✓ Faults

## System diagram

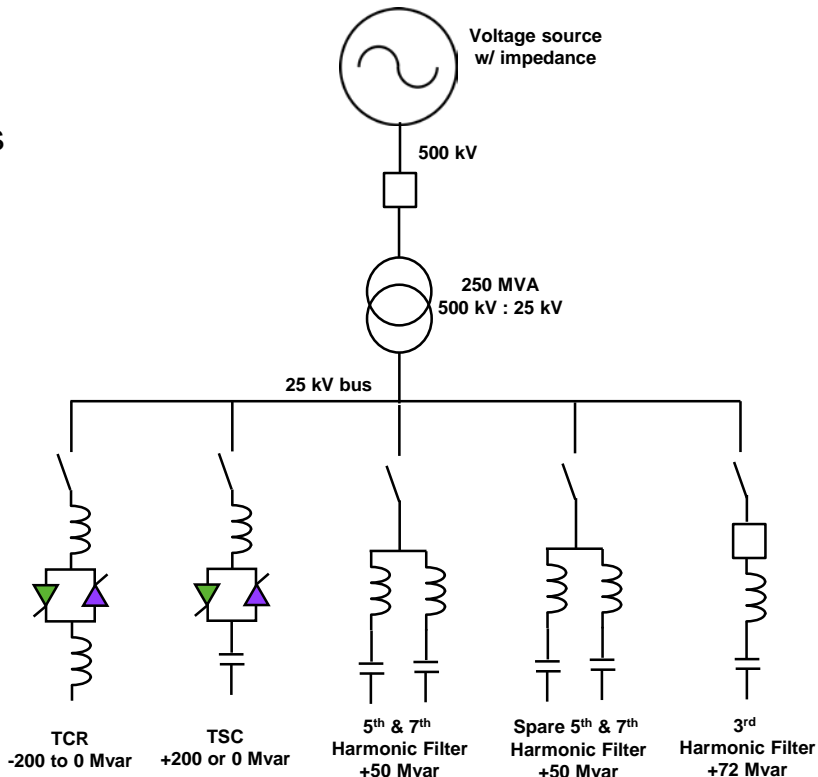


# SVC – VC Mode

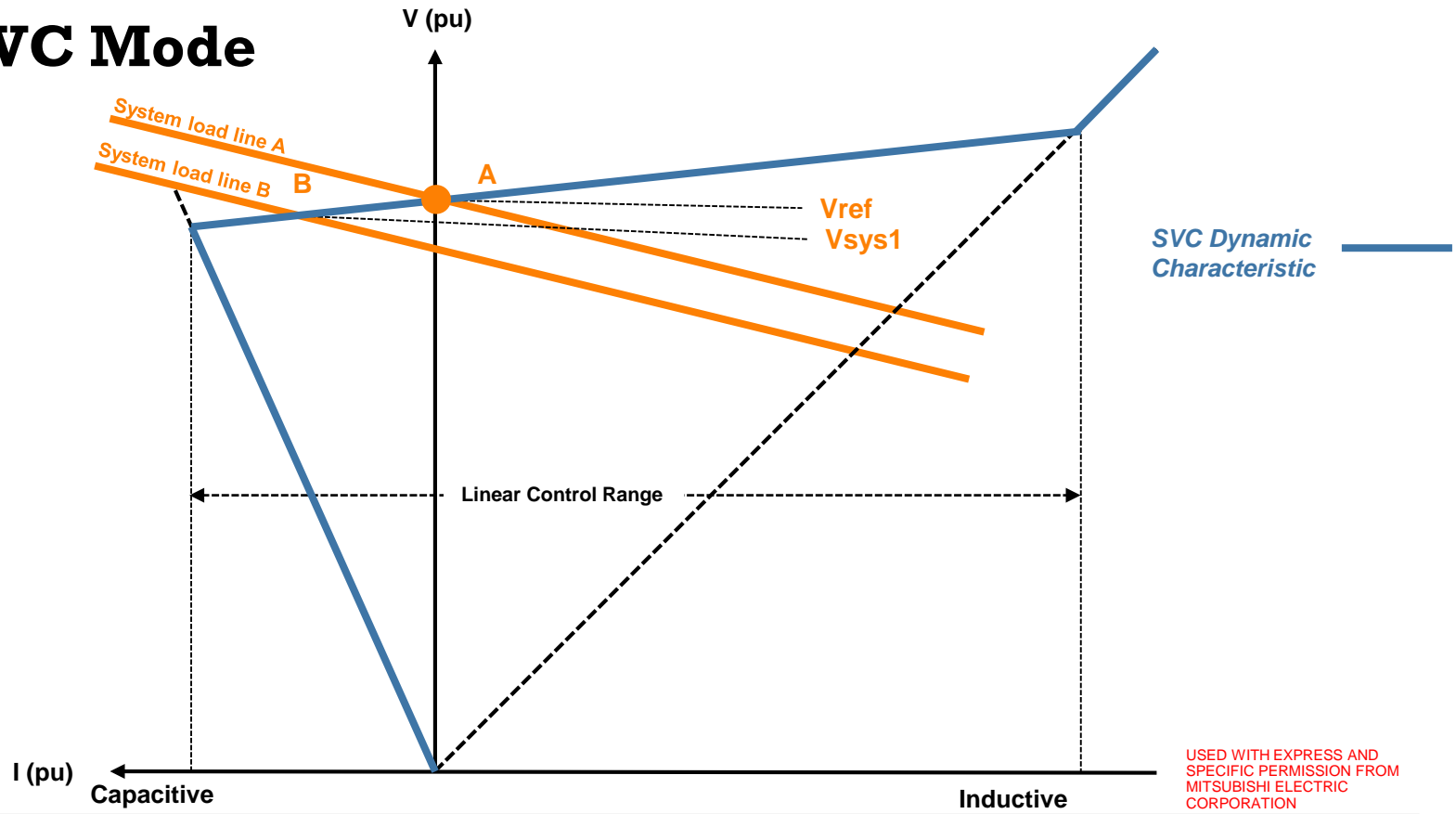

USED WITH EXPRESS AND  
SPECIFIC PERMISSION FROM  
MITSUBISHI ELECTRIC  
CORPORATION
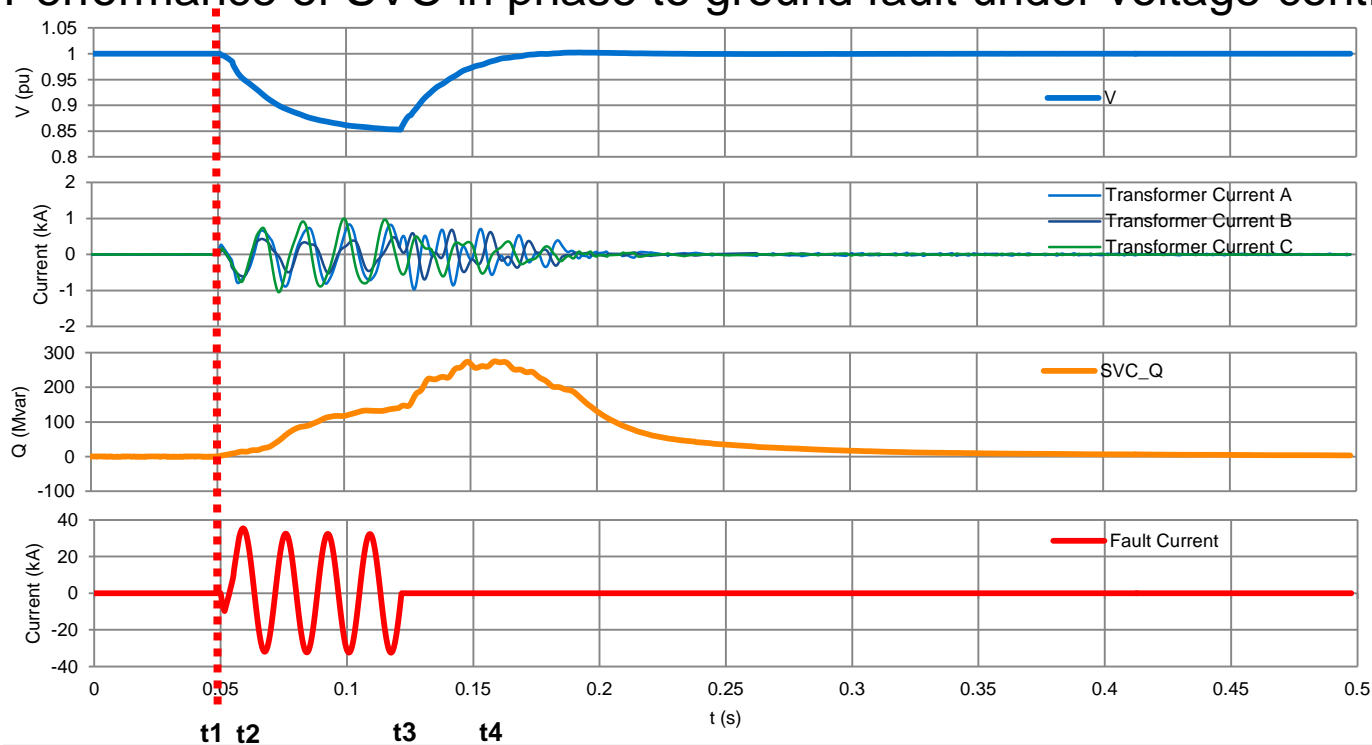
# SVC RTDS Tests

Performance of SVC in phase to ground fault under voltage-control mode



$t_1$  : L-G fault applied


$t_2$  : SVC injects  $Q$  to increase  $V$

$t_3$  : Fault is clear; SVC's  $Q$  briefly increases to regulate voltage to 1 pu

$t_4$  : SVC injects less  $Q$  as voltage is boosted to reference value




# SVC – SC Mode

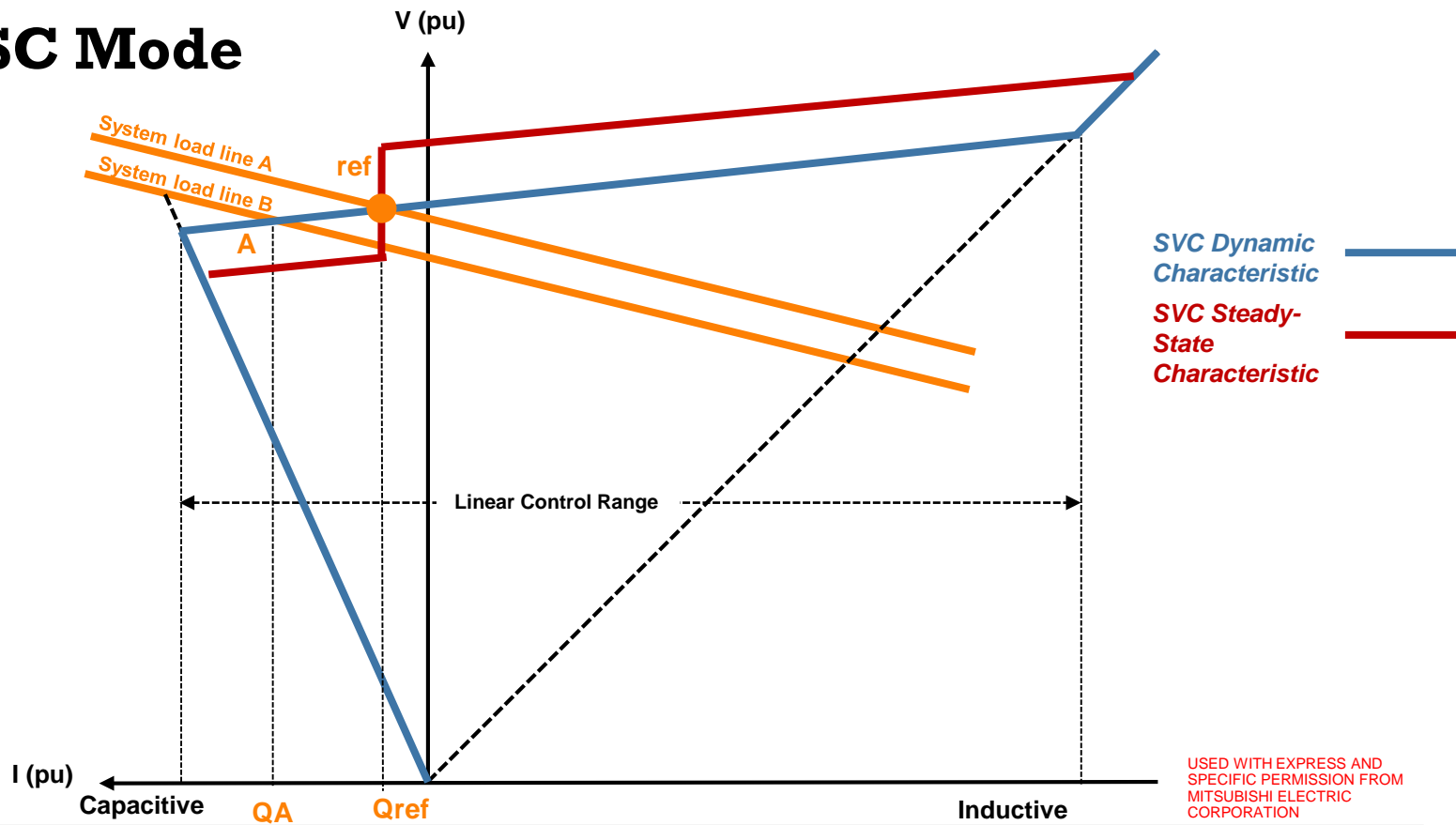
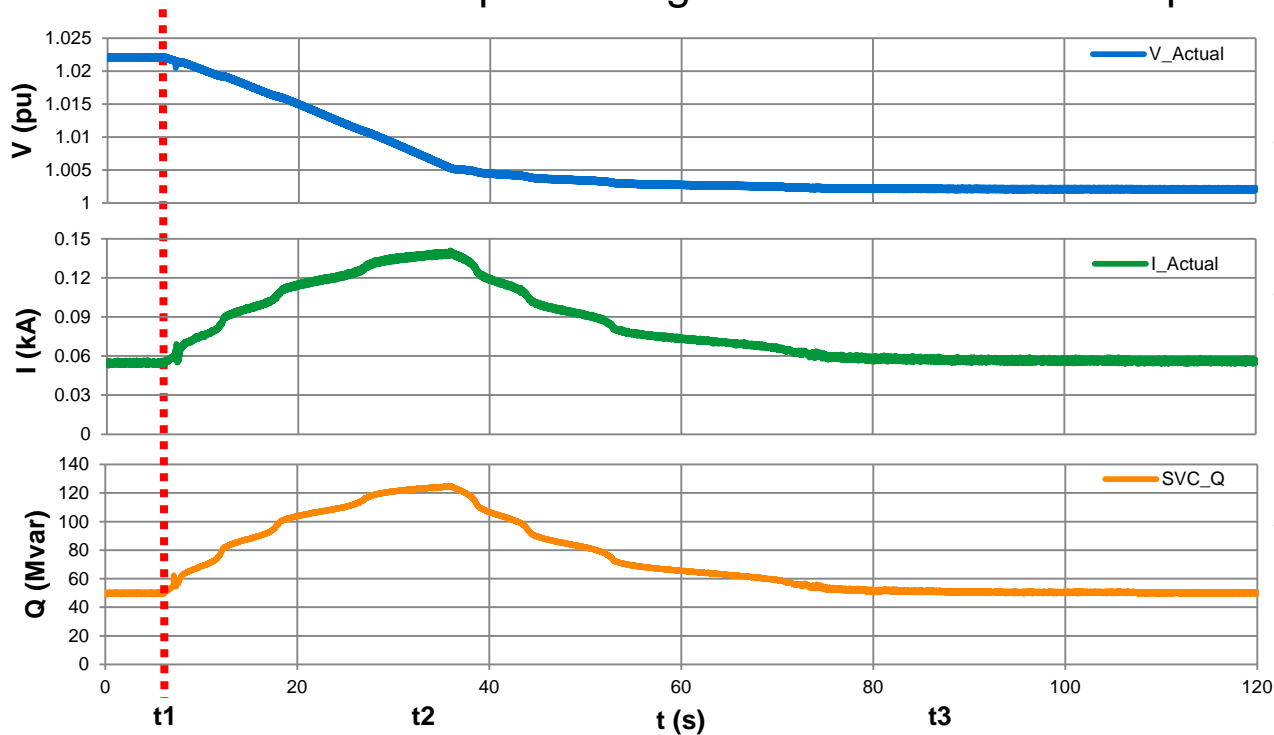
# SVC RTDS Tests

Performance of SVC in phase to ground fault under susceptance-control mode



$Q_{ref} = 50$  Mvar

$t_1$  : System voltage change;  
SVC responds dynamically


$t_2$  : System voltage settles;  
SVC's reactive power  
begins to move to  
reference value

$t_3$  : SVC's reactive power  
returns to  $Q_{ref}$  value

# RTDS Tests – Conclusions


- 1) Real STATCOM & SVC controllers can be tested using hardware-in-the-loop technology on RTDS racks.
- 2) Verified the functionality and operation of Dominion Energy's new controllers per the manufacturers' specifications.
- 3) Understand the controllers and able to predict the response of the controllers in various scenarios.
- 4) Further tested the functionality of the controllers by performing more protection sequences and various kinds of faults in the simple model.

# Interaction of the STATCOM and SVC

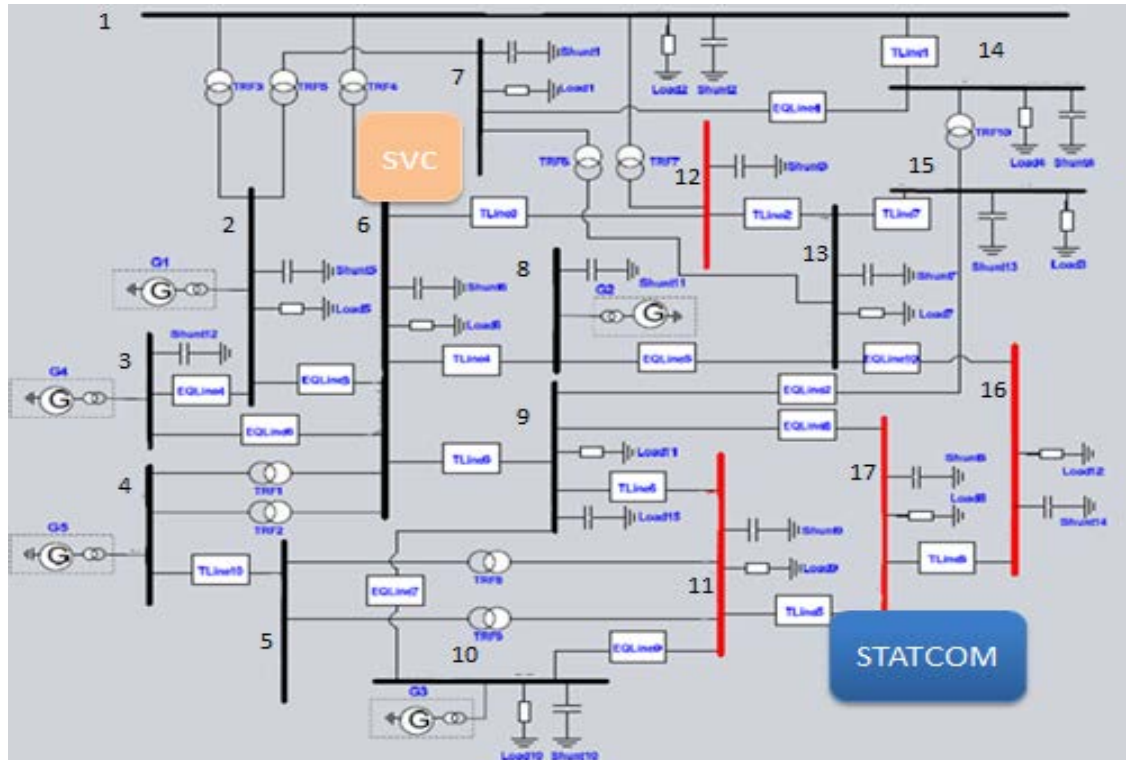
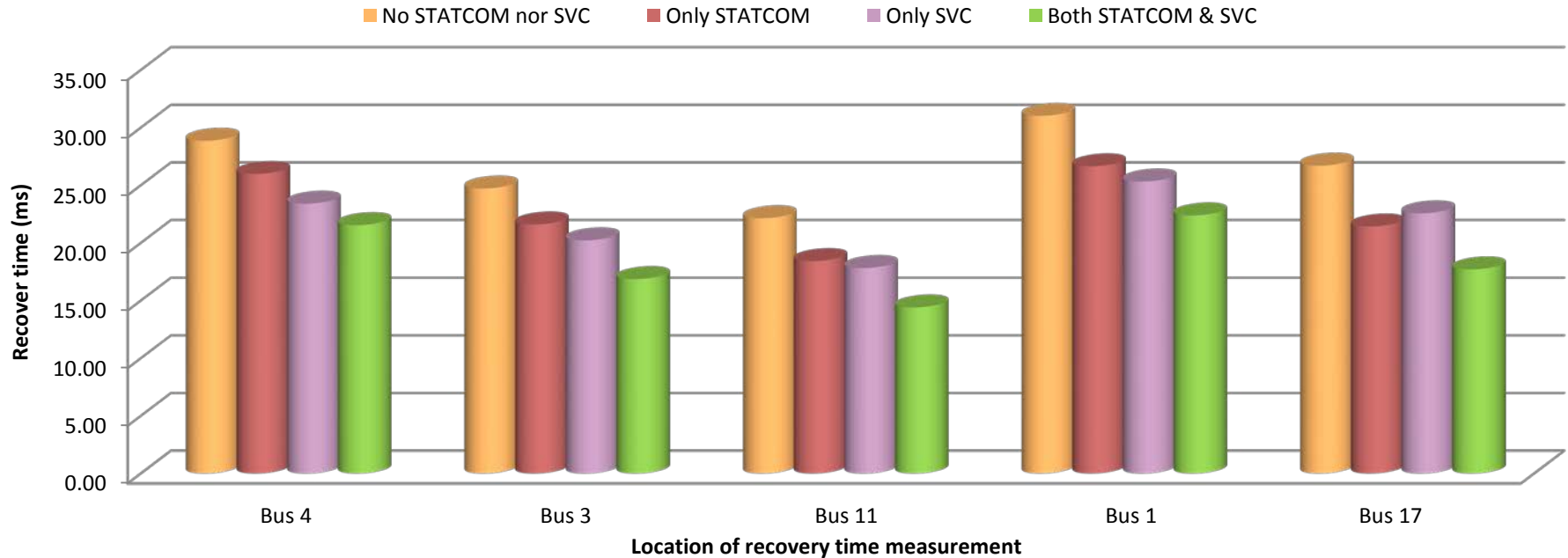
# Interaction Assessment of the STATCOM and SVC

Dynamic interaction - voltage recovery time during faults



# Progress

- ✓ Individual simulations of the real SVC and STATCOM controllers are completed using the RTDS simulation equipment and hardware-in-the-loop functionality.
- ✓ Operational and dynamic performances of the STATCOM and the SVC are tested and meet the criteria from vendor reports.
- ✓ Using an equivalent system model of an urban area, the STATCOM and the SVC controllers are successfully included in the same simulation. No negative interactions are found between the SVC and STATCOM when in close proximity.
- ✓ All tests procedures & results obtained are documented; documentation can be used for training purposes

## Future work



- (1) Build virtual STATCOM or SVC models in RTDS that emulate the real controller.
- (2) Use the virtual models to study the interactions of multiple devices in the same network.

# Thank you!







# Appendices



# Dominion Energy's SVC - Hardware

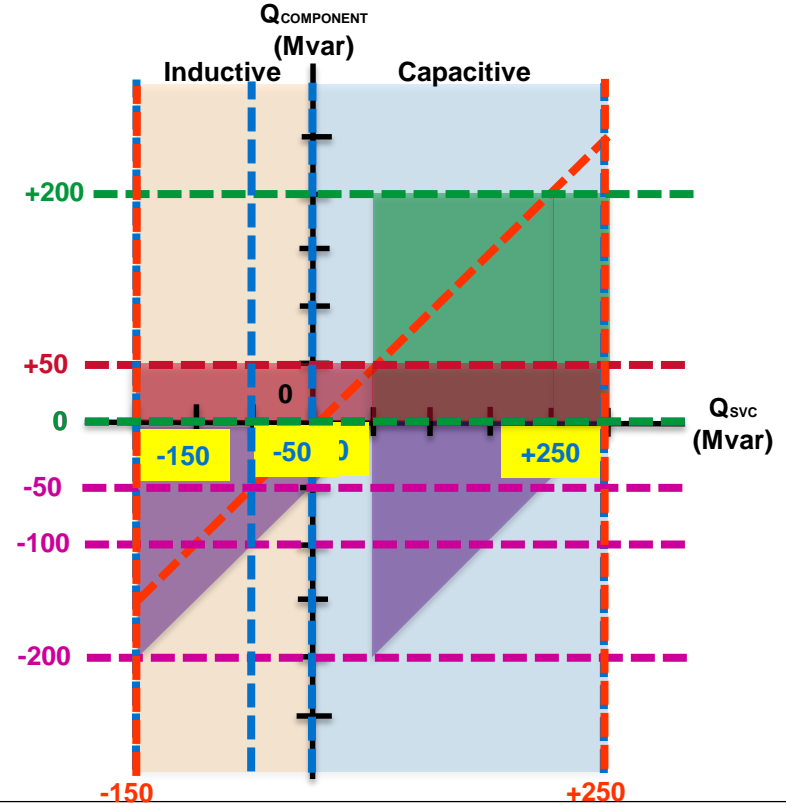
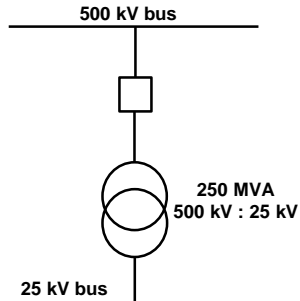

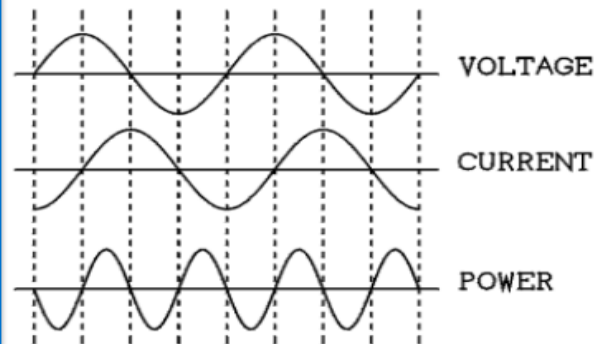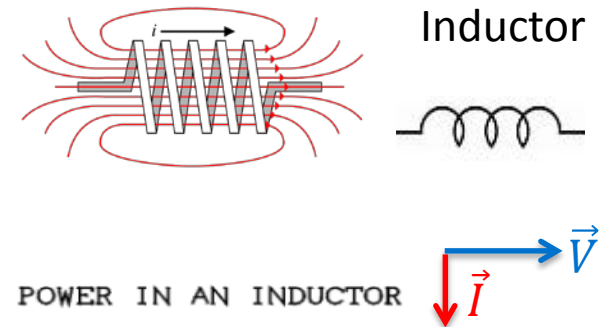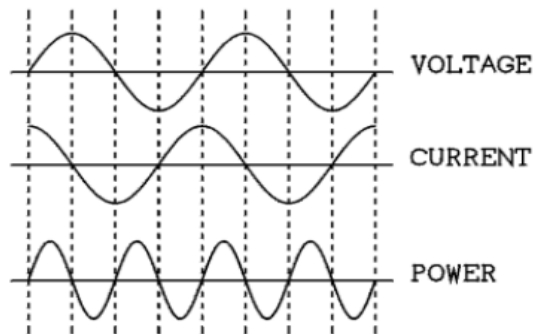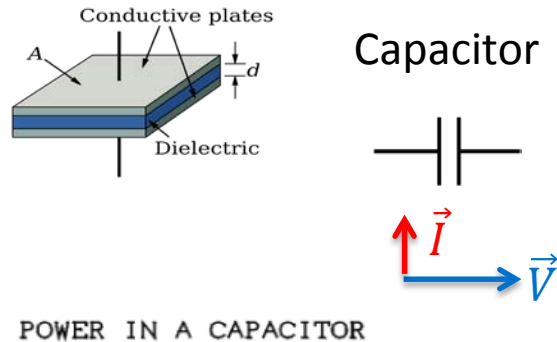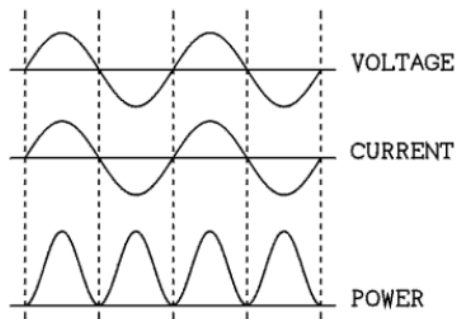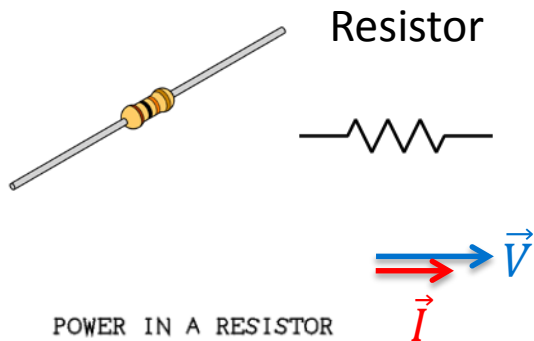
# Using Reactive Power for Voltage Regulation





# Reactive Power for Voltage Regulation

Original

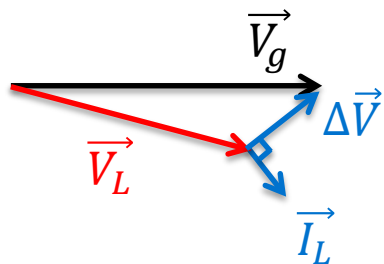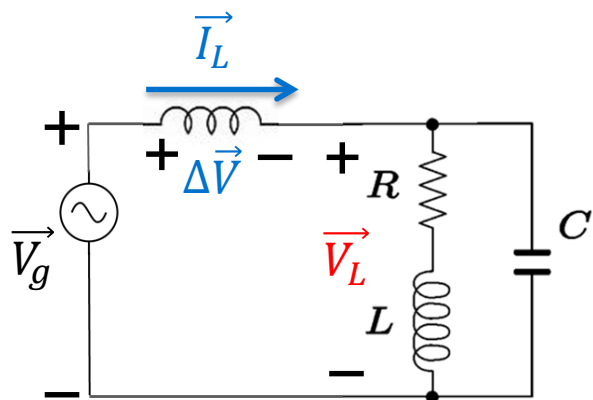

Capacitive compensation

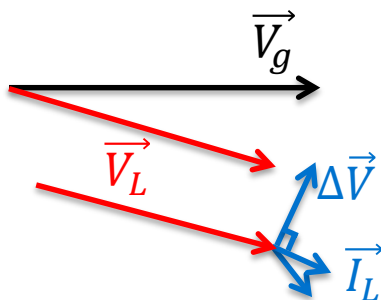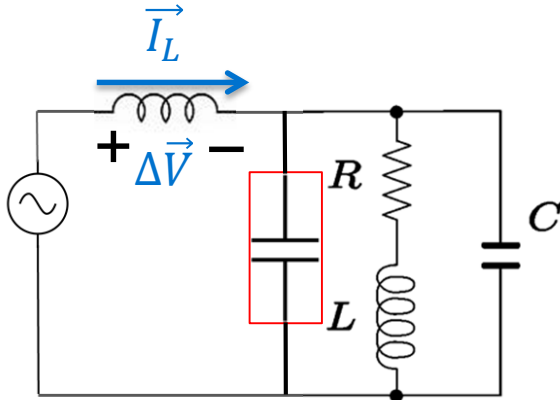

Inductive compensation

